

INDEX

A

acceptance test, 4-12
acceptance testing, 1-1
asynchronous motor, 2-29
availability, 1-3, 2-40, 3-1, 3-2, 3-6, 3-7, 3-8, 3-10, 3-12, 3-13, 4-4, 4-7

B

batteries, 1-1, 1-3, 2-20, 2-22, 2-24, 3-6, 4-1, 4-4, 4-7, 4-14, 5-16
battery, 1-1, 1-3, 2-1, 2-2, 2-3, 2-4, 2-5, 2-20, 2-21, 2-22, 2-23, 2-24, 2-25, 2-29, 2-30, 2-31, 2-32, 2-33, 2-35, 2-36, 2-38, 2-39, 3-7, 3-10, 3-11, 3-13, 3-14, 3-15, 3-16, 3-17, 3-18, 3-20, 4-1, 4-2, 4-3, 4-4, 4-6, 4-7, 4-13, 4-14, 4-15, 4-17, 4-18, 4-19, 4-20, 4-21, 5-1, 5-2, 5-3, 5-4, 5-5, 5-6, 5-7, 5-8, 5-9, 5-10, 5-11, 5-12, 5-13, 5-14, 5-15, 5-16
battery charging, 2-22
battery sizing, 3-16
bipolar transistors, 2-6, 2-7
blocking diode, 2-6

C

checklists, 1-1
controlled rectifiers, 2-9
corrective maintenance, 1-4, 5-4
crest value changes, 2-27
current limit, 2-5, 2-25, 3-16, 3-18, 4-8
cycling effects, 2-23

D

DC generators, 2-31
DC motors, 2-30, 2-31, 3-19

E

emergency power, 1-1, 2-22, 3-1, 3-6
exciters, 2-31

F

ferroresonant transformer, 2-5, 2-15, 2-17
field effect transistors (FET), 2-6, 2-7, 2-8
filtered power, 2-29
flywheel, 2-29, 2-30, 2-31, 2-32, 2-36, 2-37, 2-38, 3-18, 3-19, 3-20

G

generator, 1-2, 2-26, 2-28, 2-29, 2-30, 2-31, 2-32, 2-33, 2-36, 2-37, 2-38, 2-39, 3-6, 3-13, 3-18, 3-19, 3-20, 4-6, 4-13, 4-16, 4-17, 4-19, 4-21, 4-22
grounding, 1-1, 4-7, 4-9

H

harmonic correction techniques, 2-28
harmonic distortion, 1-1, 2-25, 3-14
harmonics, 2-1, 2-17, 2-26, 2-27, 2-28, 4-10

I

induction coupling, 2-31
induction motors, 2-30, 3-19
inrush current, 2-4, 2-5, 2-25, 2-33, 3-16, 3-18, 4-8
installation, 1-1, 2-4, 2-28, 2-33, 3-1, 3-6, 3-10, 3-11, 3-12, 3-13, 3-15, 3-16, 3-17, 3-19, 4-7, 4-11, 4-12, 4-14, 4-15, 4-17, 5-4, 5-5, 5-7, 5-8, 5-9, 5-13, 5-15
insulated gate bipolar transistor (IGBT), 2-6, 2-8, 2-14
inversion, 2-14
inverter, 1-1, 2-1, 2-2, 2-5, 2-6, 2-7, 2-14, 2-15, 2-16, 2-17, 2-18, 2-20, 2-25, 2-29, 2-30, 2-32, 2-33, 2-34, 2-35, 2-37, 2-39, 3-16, 3-17, 4-1, 4-2, 4-3, 4-4, 4-7, 4-8, 4-14, 5-3

K

kinetic battery, 2-29

L

latching devices, 2-7
lead-acid batteries, 2-20
lower power factor, 2-27

M

maintenance, 1-1, 1-3, 1-4, 2-3, 2-4, 3-11, 4-1, 4-20, 4-22, 5-1, 5-2, 5-4, 5-5, 5-7, 5-8, 5-9, 5-12, 5-14
maintenance bypass switch, 2-3
memory effect, 2-25
motor, 1-2, 2-20, 2-29, 2-30, 2-31, 2-32, 2-36, 2-37, 2-38, 2-39, 3-15, 3-18, 3-19, 3-20, 4-6, 4-13, 4-15, 4-16, 4-19

N

neutral harmonic behavior, 2-27
nickel-cadmium batteries, 2-20, 2-22, 5-6, 5-15
noise feedback, 2-28
nonlinear loads, 2-25, 2-32

O

operations, 1-1

P

power, 1-1, 1-2, 1-3, 1-4, 2-1, 2-2, 2-3, 2-4, 2-6, 2-7, 2-8, 2-9, 2-14, 2-15, 2-18, 2-20, 2-21, 2-22, 2-23, 2-25, 2-26, 2-27, 2-28, 2-29, 2-30, 2-31, 2-32, 2-33, 2-34, 2-35, 2-36, 2-37, 2-38, 2-39, 2-40, 3-1, 3-2, 3-6, 3-7, 3-8, 3-9, 3-10, 3-13, 3-15, 3-16, 3-17, 3-18, 3-19, 3-20, 4-1, 4-2, 4-6, 4-7, 4-8, 4-9, 4-10, 4-11, 4-12, 4-13, 4-14, 4-15, 4-16, 4-17, 4-21, 5-1, 5-3, 5-4, 5-5, 5-13

power diodes, 2-9

power requirements, 3-6

preventive maintenance, 1-4, 5-1, 5-5

probability, 3-8, 5-2

protective devices, 1-3, 3-16, 4-7, 4-8, 4-9

pulse width modulation (PWM), 2-5, 2-15, 2-16, 2-17

R

rectification, 2-8

rectifier, 1-1, 2-1, 2-2, 2-5, 2-6, 2-8, 2-9, 2-10, 2-11, 2-12, 2-25, 2-26, 2-29, 2-32, 2-33, 2-35, 2-36, 2-39, 4-3, 4-17, 4-20, 4-22, 5-3, 5-4, 5-6, 5-8, 5-9, 5-10, 5-13, 5-15, 5-16

reliability, 2-20, 2-21, 2-28, 2-33, 2-34, 2-35, 2-36, 2-37, 2-38, 2-39, 2-40, 3-1, 3-7, 3-8, 3-9, 3-10, 3-11, 3-20, 5-1, 5-2, 5-8

ripple currents, 2-25

rotary UPS, 1-1, 1-2, 1-4, 2-29, 2-30, 2-31, 2-32, 2-33, 2-36, 2-37, 3-13, 3-18, 3-20, 4-6, 4-7, 4-13, 5-5

S

safety, 3-6, 4-22, 4-23, 5-1, 5-5, 5-15, 5-16

SCR, 2-1, 2-3, 2-4, 2-6, 2-7, 2-14, 2-15, 2-16, 2-17, 2-18, 2-19, 4-20, 4-21

shielding, 1-4, 4-7, 4-10

single-phase uncontrolled rectifiers, 2-8

sizing selection, 1-1

standby power, 1-1, 3-1, 3-6

static switch, 1-2, 2-1, 2-2, 2-20, 2-33, 2-35, 2-36, 2-39, 4-8, 4-17, 4-19

static transfer switch, 2-18, 2-20, 2-33, 2-34, 2-36, 3-16, 3-18, 4-8

static UPS, 1-1, 1-2, 2-1, 2-6, 2-14, 2-20, 2-22, 2-25, 2-26, 2-31, 2-32, 2-33, 2-35, 2-36, 2-39, 2-40, 3-13, 3-15, 3-16, 3-17, 3-18, 4-1, 4-2, 4-7, 5-5

synchronous motor, 2-29, 2-37, 4-6

system rating, 1-1, 3-18

T

testing, 1-3, 1-4, 4-1, 4-11, 4-13, 4-15, 4-16, 5-5, 5-6

three-phase uncontrolled rectifiers, 2-8

transistors, 2-6, 2-7, 2-8, 2-15

troubleshooting, 1-1, 3-11, 4-23, 5-4, 5-5, 5-16

U

unbalanced load, 2-32

V

valve regulated lead acid batteries (VRLA), 2-21
voltage tapping, 2-23

W

walk-in time, 2-5

Z

zero crossing increases, 2-28